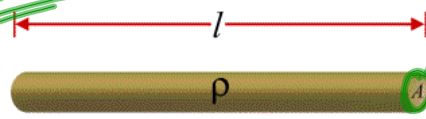


Resistance of a Wire

Pink Worksheet



$$A = \pi r^2$$

Greek letter ρ = rho = resistivity value

$$R = \frac{\rho l}{A}$$

① Long skinny wire.

$\uparrow L \therefore \uparrow R$

$\downarrow A \therefore \uparrow R$

②

$$R = \frac{\rho L}{A} \quad \uparrow L 3x \therefore \uparrow R 3x$$

③

$\uparrow A 3x \therefore R \downarrow \frac{1}{3}x$

④

$$R = \frac{\rho L}{A} \quad R = \frac{\rho L}{\pi r^2}$$

$A = \pi r^2$

$r \downarrow \frac{1}{2}x$

$\therefore R \uparrow 4x$

⑤


$$R = \frac{\rho L}{A}$$

$L \downarrow \frac{1}{2}x \therefore R \downarrow \frac{1}{2}x$

⑥

$$R = \frac{\rho L}{A} \quad A \uparrow 2x \therefore R \downarrow \frac{1}{2}x$$

⑦

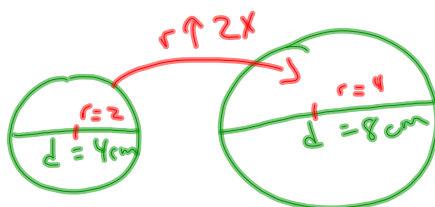

$$R = \frac{\rho L}{\pi r^2} \quad r \uparrow 2x \therefore R \downarrow \frac{1}{4}x$$

⑧

$$R = \frac{P L}{A}$$

$$9_m \rightarrow 3_m$$

$$\frac{A}{B} = \frac{3}{9} = \frac{1}{3}$$

$$L \downarrow \frac{1}{3} \times$$

$$\therefore R \downarrow \frac{1}{3} \times$$

⑨

For very $\uparrow I$, need very $\downarrow R$
 as per $I = \frac{V}{R}$

For very $\downarrow R$, need $\uparrow A$
 as per $R = \frac{P L}{A}$.

* For $\uparrow I$ need $\uparrow A$.

⑩

Short as possible

⑪

 $\downarrow r \frac{1}{3} \times$

$$R = \frac{\rho L}{\pi r^2}$$

$$R \uparrow 9 \times$$

$$I = \frac{V}{R}$$

$$I \downarrow \frac{1}{9} \times$$

⑫ If you use a wire that's too thin, the resistance will be too high. This could start a fire. Also, it would $\downarrow I$ so appliance wouldn't operate properly.

Coulomb's Law

$$F = k \frac{Q_1^{x3} Q_2^{x2}}{d^2}$$

$F =$ Force between charges

$Q_1 =$
 $Q_2 =$ } Two different point charges in Coulombs.
 -1 C

• \rightarrow
 Point charge
 $Q_1 = 1.2 \times 10^{-2} \text{ C}$

$Q_2 = 1.8 \times 1$

$\uparrow Q_1 \ 2x \therefore F \uparrow 2x$

$\uparrow d \ 3x \therefore d \downarrow \frac{1}{9} x$

$$F = \frac{k Q_1 Q_2}{d^2}$$

① a) $Q_1 \uparrow 2X \therefore \boxed{F \uparrow 2X}$

b) $d \uparrow 2X \therefore \boxed{F \downarrow \frac{1}{4}X}$

c) $Q_1 \uparrow 2X \quad Q_2 \uparrow 2X \quad \boxed{F \uparrow 4X}$

② a) $d \uparrow 4X \therefore F \downarrow \frac{1}{16}X$


b) $d \downarrow \frac{1}{2}X \therefore F \uparrow 4X$

Series Circuit

Parallel Circuit

resistor $\Sigma = V_1 + V_2 + V_3$
 $6V$

$$\Sigma = V_1 = V_2 = V_3$$

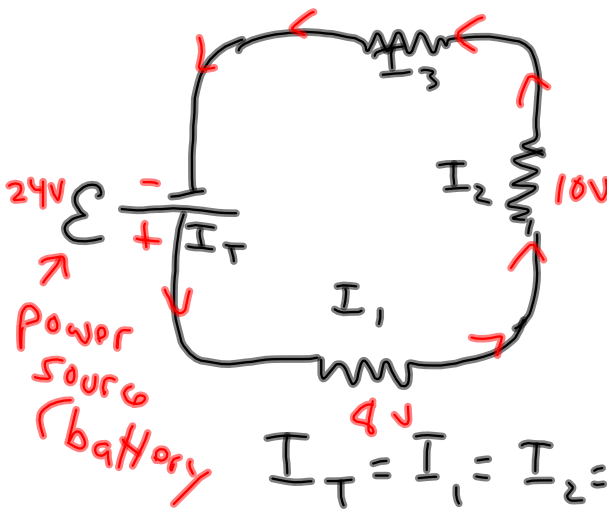

$$I_T = I_1 = I_2 = I_3$$

Voltage is same in resistors that are in parallel

actual current : flow of e^- 's from - to +

conventional current : flow of + particles from + to -

→ We will use this

Series

$$I_T = I_1 = I_2 = I_3$$


$$\mathcal{E} = V_1 + V_2 + V_3$$

Parallel

$$\mathcal{E} = V_1 = V_2 = V_3$$

$$I_T = I_1 + I_2 + I_3$$

①

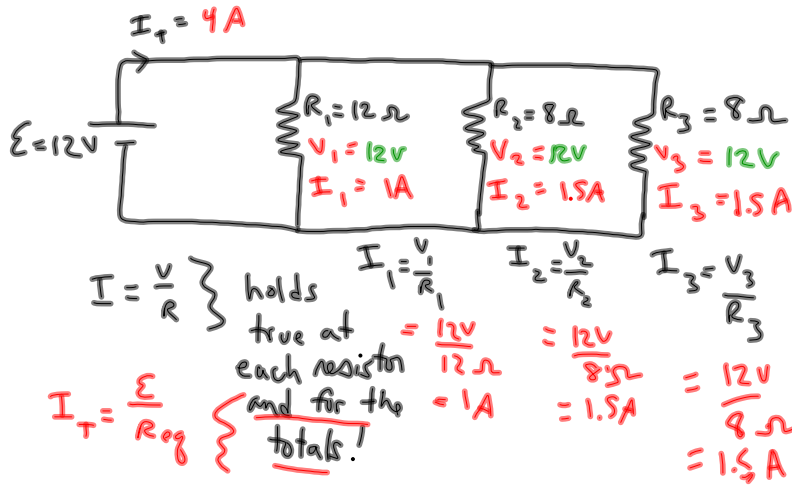

R_{eq} = "equivalent resistance"

$$\frac{1}{R_{eq}} = \frac{1}{R_1} + \frac{1}{R_2} + \frac{1}{R_3}$$

$$\frac{1}{R_{eq}} = \frac{1}{12} + \frac{1}{8} + \frac{1}{8}$$

$$\frac{1}{R_{eq}} = 0.0833 + 0.125 + 0.125$$

$$\frac{1}{R_{eq}} = 0.333$$

$$\frac{1}{x} = \frac{0.333}{1}$$

$$\frac{x}{1} = \frac{1}{0.333}$$

$$x = 3\Omega$$

$$R_{eq} = \frac{1}{0.333} = 3\Omega$$


$$x^{-1}$$

$$\frac{1}{x}$$

OR

$$I_T = \frac{\mathcal{E}}{R_{eq}}$$

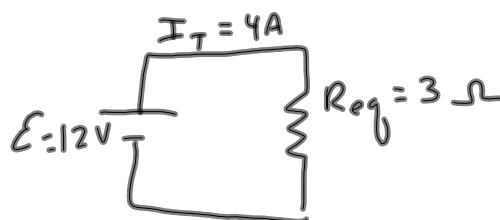
$$R_{eq} = \frac{\mathcal{E}}{I_T} = \frac{12V}{4A} = 3\Omega$$



2.

$$I_T = I_1 + I_2 + I_3 + I_4$$

$$= 11.7 \text{ A}$$

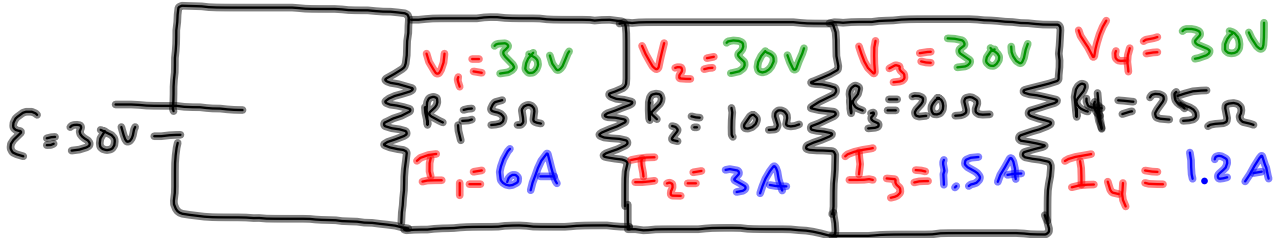

$$I_1 = \frac{V_1}{R_1}$$

$$I_2 = \frac{V_2}{R_2}$$



OR

$$\frac{1}{R_{eq}} = \frac{1}{R_1} + \frac{1}{R_2} + \frac{1}{R_3} + \frac{1}{R_4}$$

$$R_{eq} = \frac{\mathcal{E}}{I_T}$$

$$\frac{1}{R_{eq}} = \frac{1}{5} + \frac{1}{10} + \frac{1}{20} + \frac{1}{25}$$


$$\frac{1}{R_{eq}} = 0.2 + 0.1 + 0.05 + 0.04$$

$$\frac{1}{R_{eq}} = 0.39$$

$$R_{eq} = \frac{1}{0.39} = 2.56 \Omega$$

White : Parallel Circuits

$$I_T = 4A$$

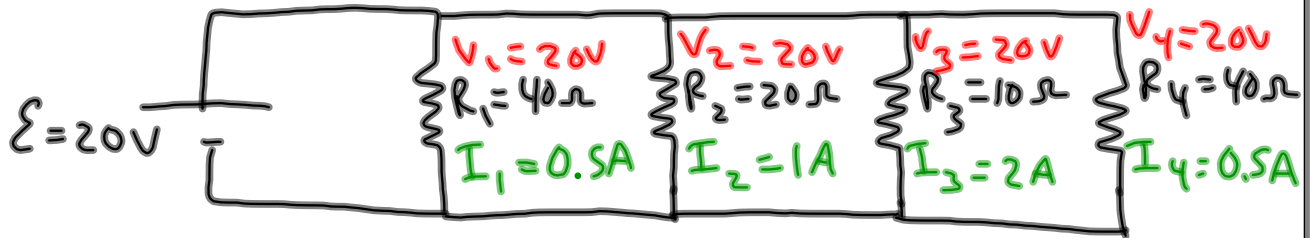

$$\frac{1}{R_{eq}} = \frac{1}{R_1} + \frac{1}{R_2} + \frac{1}{R_3} + \frac{1}{R_4}$$

$$\frac{1}{R_{eq}} = \frac{1}{40} + \frac{1}{20} + \frac{1}{10} + \frac{1}{40}$$

$$\frac{1}{R_{eq}} = 0.025 + 0.05 + 0.1 + 0.025$$

$$\frac{1}{R_{eq}} = 0.2$$

$$R_{eq} = \frac{1}{0.2} = 5\Omega$$