

Q = charge (amount of negativity)

$$Q = I t$$

\nearrow Charge in A·h (ampere-hours)
 \uparrow current in A (amps)
 \nwarrow time in hours

① $Q_{\text{initial}} = 90 \text{ A}\cdot\text{h}$

$$\begin{aligned}
 Q_{\text{used up}} &= I t \\
 &= (15 \text{ A})(5.5 \text{ h}) \\
 &= 82.5 \text{ A}\cdot\text{h}
 \end{aligned}$$

$$\begin{aligned}
 Q_{\text{left}} &= 90 \text{ A}\cdot\text{h} - 82.5 \text{ A}\cdot\text{h} \\
 &= 7.5 \text{ A}\cdot\text{h}
 \end{aligned}$$

$$\begin{aligned}
 35 &\div 3600 \\
 &= 0.00083 \text{ h}
 \end{aligned}$$

$$\begin{aligned}
 Q_{\text{needed}} &= I t \\
 \text{for 1 start-up} &= (400 \text{ A})(0.00083 \text{ h}) \\
 &= 0.33 \text{ A}\cdot\text{h}
 \end{aligned}$$

Yes the car will start
 $Q_{\text{needed}} < Q_{\text{left}}$

Ohm's Law


$$V = IR$$

$$\frac{V}{R} = \frac{IR}{R}$$

$$\frac{V}{I} = \frac{IR}{I}$$

$$I = \frac{V}{R}$$

$$R = \frac{V}{I}$$

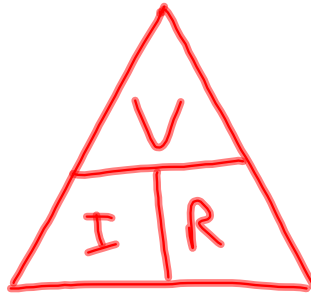

$$\textcircled{1} \quad V = 6V$$
$$I = 0.33A$$
$$R = ?$$

$$R = \frac{V}{I} = \frac{6V}{0.33A} = \boxed{18.18 \Omega}$$

$$\textcircled{2} \quad V = 120V$$
$$I = ?$$
$$R = 300 \Omega$$

$$I = \frac{V}{R} = \frac{120V}{300 \Omega} = \underline{\underline{0.4A}}$$

$$1000mA = 1A$$

$$mA \rightarrow A$$
$$\div 1000$$

③

$$V = 9V$$

$$I = 0.5A$$

$$R = ?$$

$$R = \frac{V}{I} = \frac{9V}{0.5A}$$

$$= \boxed{18\Omega}$$

④

$$I = 1.7A$$

$$R = 71\Omega$$

$$V = ?$$

$$V = IR$$

$$= (1.7A)(71\Omega)$$

$$= \boxed{120.7V}$$

$$\textcircled{5} \quad V = 240\text{V}$$
$$R = 113 \Omega$$
$$I = ?$$

$$I = \frac{V}{R} = \frac{240\text{V}}{113 \Omega} = \boxed{2.12 \text{A}}$$

$$\textcircled{6} \quad V = 12\text{V}$$
$$I = 2.5\text{A}$$
$$R = ?$$

$$R = \frac{V}{I} = \frac{12\text{V}}{2.5\text{A}} = \boxed{4.8 \Omega}$$

$$\begin{aligned} \textcircled{7} \quad V &= 240 \text{ V} \\ R &= 135 \, \Omega \\ I &= ? \end{aligned}$$

$$I = \frac{V}{R} = \frac{240 \text{ V}}{135 \, \Omega} = \boxed{1.78 \text{ A}}$$

$$\begin{aligned} \textcircled{8} \quad R &= 40 \, \Omega \\ I &= 15 \text{ A} \\ V &= ? \end{aligned}$$

$$\begin{aligned} V &= IR \\ &= (15 \text{ A})(40 \, \Omega) \\ &= \boxed{600 \text{ V}} \end{aligned}$$

$$\textcircled{9} \quad I = 9 \text{ mA} = \boxed{0.009 \text{ A}}$$

$\xrightarrow{\div 1000}$

$$V = 3 \text{ V}$$

$$R = \frac{V}{I} = \frac{3 \text{ V}}{0.009 \text{ A}} = \boxed{333.33 \Omega}$$

$\textcircled{10}$

$$R = 9 \Omega$$

$$I = 450 \text{ mA} = 0.45 \text{ A}$$

$$V = IR = (0.45 \text{ A})(9 \Omega) = \boxed{4.05 \text{ V}}$$

$$I = \frac{V}{R}$$

$$R = 6 \Omega$$

$$I = \frac{V}{R} \times 2$$

- a) 12V $I = 2A$
- b) 24V $I = 4A$
- c) 36V $I = 6A$
- d) 48V $I = 8A$
- e) 6V $I = 1A$
- f) 3V $I = 0.5A$

V is directly proportional to I.

$\uparrow V \ 2x \therefore \uparrow I \ 2x$	$\downarrow V \ \frac{1}{2}x \therefore \downarrow I \ \frac{1}{2}x$
$\uparrow V \ 3x \therefore \uparrow I \ 3x$	$\downarrow V \ \frac{1}{3}x \therefore \downarrow I \ \frac{1}{3}x$
$\uparrow V \ 10x \therefore \uparrow I \ 10x$	$\downarrow V \ \frac{1}{5}x \therefore \downarrow I \ \frac{1}{5}x$

e.g. Start with $V = 15V$, then switch to V of $21V$.

Before $V = 15V$ After $V = 21V$

$$\frac{A}{B} = \frac{21 \div 3}{15 \div 3} = \frac{7}{5} \quad V \uparrow \frac{7}{5}x \therefore I \uparrow \frac{7}{5}x$$

If a Voltage is changed from $12V \rightarrow 20V$, by how many times will the current change?

$$12 \times \frac{5}{3} = 20$$

$$V \uparrow \frac{5}{3}x$$

$$I \uparrow \frac{5}{3}x$$

$$\frac{A}{B} = \frac{20 \div 4}{12 \div 4} = \frac{5}{3}$$

If V is changed from $32V$ to $24V$, how would I be affected?


$$V \downarrow \frac{3}{4}x$$

$$\frac{A}{B} = \frac{24 \div 8}{32 \div 8} = \frac{3}{4}$$

$$\therefore I \downarrow \frac{3}{4}x$$

$$32 \times \frac{3}{4} = \frac{96}{4} = 24$$

$$V = 36V \quad I = \frac{V}{R}$$

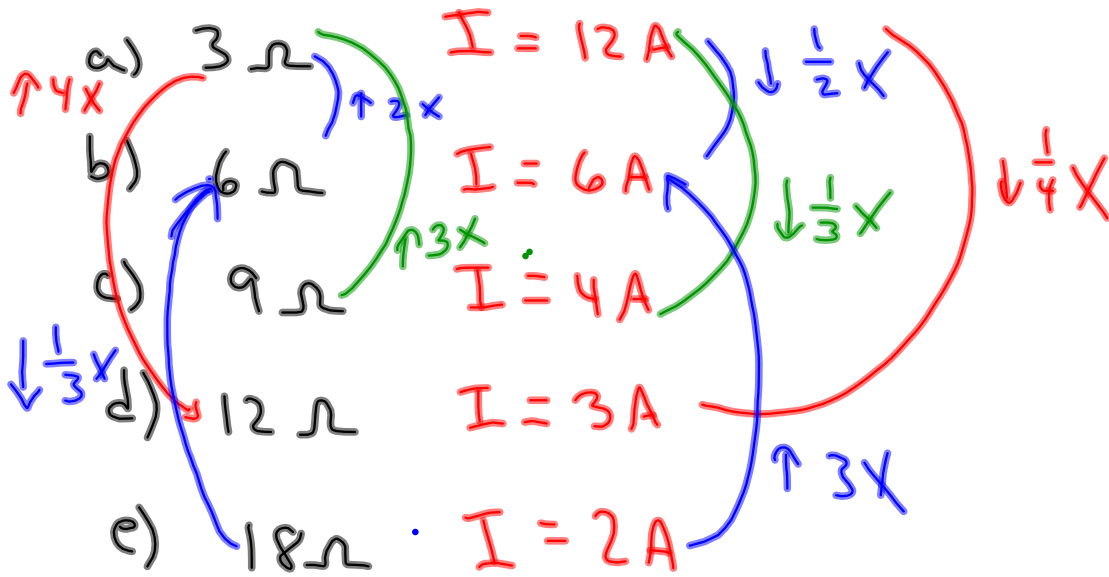

R & I are indirectly proportional.

$$\uparrow R \therefore \downarrow I$$

$$\downarrow R \therefore \uparrow I$$

By "flip" ams $\square = \frac{\square^2 \square^3}{\square \square}$

$$I = \frac{V}{R} \quad \frac{V}{R} \quad \frac{1}{2 \cdot 2} \quad \frac{1}{4} \quad \frac{1}{6} \quad \frac{1}{8}$$

If R is changed from $15\ \Omega$ to $36\ \Omega$, how will I be affected? $I = \frac{V}{R}$ ①

(A) $\frac{36}{15} \div 3$ (B) $\frac{12}{5}$
 $R \uparrow \frac{12}{5} \times \therefore I \downarrow \frac{5}{12} \times$
 ①

If R is changed from $120\ \Omega$ to $34\ \Omega$, how is I affected. ①

$I = \frac{V}{R}$ $R \downarrow \frac{17}{60} \times \therefore I \uparrow \frac{60}{17} \times$ $\frac{34}{120} \div 2 = \frac{17}{60}$

(11)

(B) 12V → 9V (A)

$$\frac{A}{B} = \frac{9 \div 3}{12 \div 3} = \frac{3}{4}$$

1 mark

$$I = \frac{V}{R}$$

$V \downarrow \frac{3}{4} \times \therefore I \downarrow \frac{3}{4} \times$
 1 mark 1 mark

(12)

(B) 9V → 12V (A)

$$\frac{A}{B} = \frac{12 \div 3}{9 \div 3} = \frac{4}{3}$$

= 1.33

$$I = \frac{V}{R}$$

$V \uparrow \frac{4}{3} \times \therefore I \uparrow \frac{4}{3} \times$
 (1) (1)

(13) $\overset{B}{6V} \rightarrow \overset{A}{9V}$

$$\frac{A}{B} = \frac{9 \div 3}{6 \div 3} = \frac{3}{2}$$

① $I = \frac{V}{R}$ $V \uparrow \frac{3}{2} \times \therefore I \uparrow \frac{3}{2} \times$ 2 marks

(14) $\overset{B}{12V} \rightarrow \overset{A}{6V}$ $I = \frac{V}{R}$

$$\frac{A}{B} = \frac{6 \div 6}{12 \div 6} = \frac{1}{2}$$

$V \downarrow \frac{1}{2} \times \therefore I \downarrow \frac{1}{2} \times$

(15) $\overset{B}{9V} \rightarrow \overset{A}{6V}$

$$\frac{A}{B} = \frac{6 \div 3}{9 \div 3} = \frac{2}{3}$$

$I = \frac{V}{R}$

$V \downarrow \frac{2}{3} \times \therefore I \downarrow \frac{2}{3} \times$

(16) $3V \rightarrow 9V$
 $V \uparrow 3X \therefore I \uparrow 3X$

$I = \frac{V}{R}$

(17) $I = \frac{V}{R}$

$R \uparrow 3X \therefore I \downarrow \frac{1}{3} X$

(18)

$$I = \frac{V}{R}$$

 $R \uparrow 2X$ $\therefore I \downarrow \frac{1}{2} X$

(19)

$$I = \frac{V}{R}$$

 $R \downarrow \frac{1}{2} X \therefore I \uparrow 2X$

(20)

 $\overset{B}{20\Omega} \rightarrow \overset{A}{30\Omega}$

$$\frac{A}{B} = \frac{30}{20} = \frac{3}{2}$$

$$I = \frac{V}{R}$$

 $R \uparrow \frac{3}{2} X$ $\therefore I \downarrow \frac{2}{3} X$