
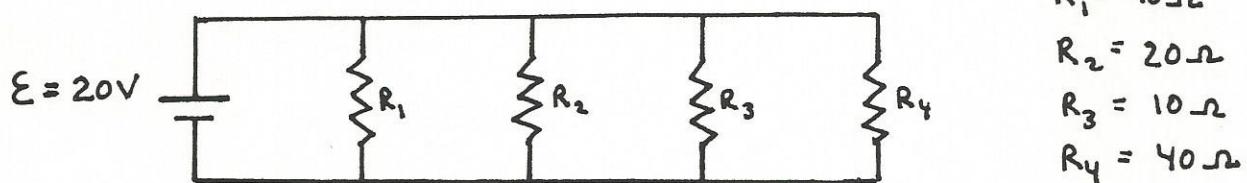


Physical Science Worksheet : Parallel Circuits

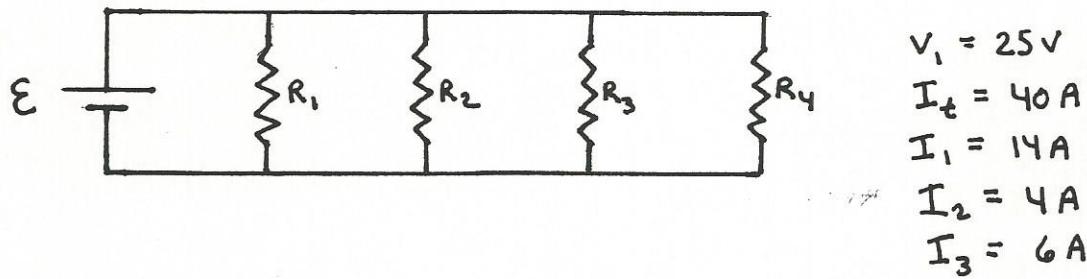
1. Do a complete analysis of the following circuit after drawing the corresponding simple equivalent circuit.



2. Do a complete analysis of the following circuit after drawing the corresponding simple equivalent circuit.




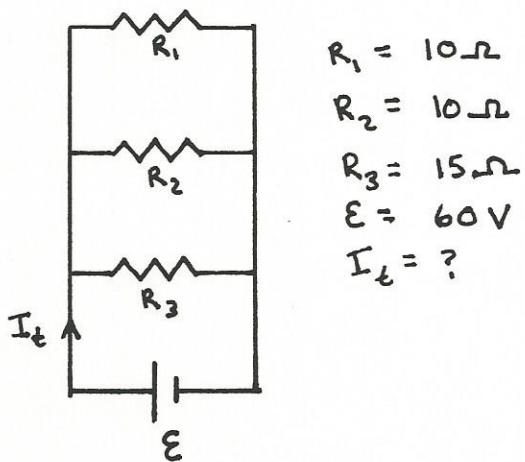3. In the circuit diagram below, determine the value of I_t , the current supplied by the source. Your answer must indicate the formulas used and must include all calculations, including a clear indication of the units of measure throughout the calculations.




$$\begin{aligned}R_1 &= 10\Omega \\R_2 &= 10\Omega \\R_3 &= 15\Omega \\\epsilon &= 60V \\I_t &=?\end{aligned}$$

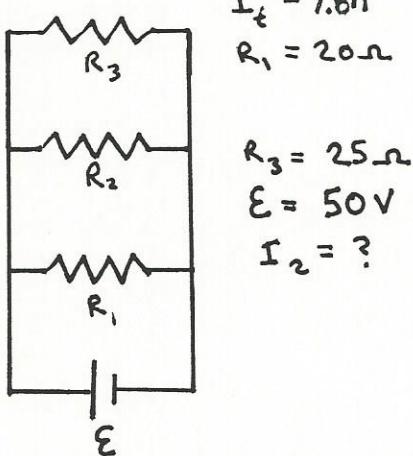4. In the following diagram, determine I_2 , the current flowing through R_2 . Include all calculations, formulas + units.



$$\begin{aligned}I_t &= 7.8A \\R_1 &= 20\Omega \\R_3 &= 25\Omega \\\epsilon &= 50V \\I_2 &=?\end{aligned}$$

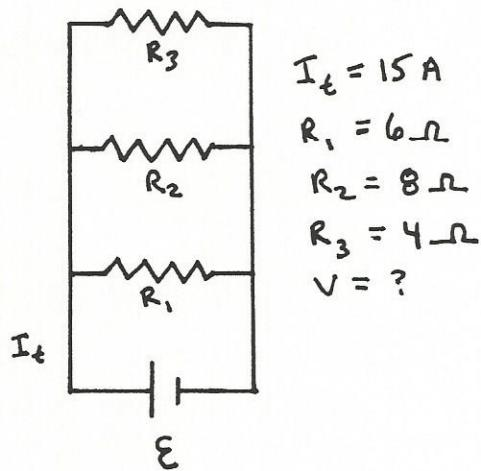5. In the circuit diagram given below, determine the value of V the electromotive force. You must include formulas, calculations, and units.



$$I_t = 15 \text{ A}$$

$$R_1 = 6 \Omega$$

$$R_2 = 8 \Omega$$

$$R_3 = 4 \Omega$$

$$V = ?$$

6. a) Determine the total resistance of the resistors in the circuit shown below.

b) What is the voltage supplied by the power source?

